

Session 6

-

Display devices, LCD display

Author: Guillermo Cortés Orellana

Teacher: Tomáš Frýza

Lab assignment

1. Preparation tasks

- Table with LCD signals

| LCD signal (s) | AVR pin(s) | Description |
|----------------|--------------------|---|
| RS | PB0 | Register selection signal. Selection between Instruction register (RS=0) and Data register (RS=1) |
| R/W | GND | Pin writing/reading to/from - LCD |
| E | PB1 | Enabling pin. When this pin is set to logical low, the LCD does not care what is happening with R/W, RS, and the data bus lines. When this pin is set to logical high, the LCD is processing the incoming data |
| D[3:0] | - | We won't use them. They would only be used if we worked in 8 bits mode |
| D[7:4] | PD4, PD5, PD6, PD7 | Four high order bidirectional tristate data bus pins. Used for data transfer and receive between the MPU and the LCD |

- ASCII values

| Representation | Binary | Decimal | Hexadecimal |
|----------------|-----------|---------|-------------|
| A | 0100 0001 | 65 | 41 |
| B | 0100 0010 | 66 | 42 |
| C | 0100 0011 | 67 | 43 |
| D | 0100 0100 | 68 | 44 |
| E | 0100 0101 | 69 | 45 |
| F | 0100 0110 | 70 | 46 |
| G | 0100 0111 | 71 | 47 |
| H | 0100 1000 | 72 | 48 |
| I | 0100 1001 | 73 | 49 |
| J | 0100 1010 | 74 | 4A |
| K | 0100 1011 | 75 | 4B |
| L | 0100 1100 | 76 | 4C |
| M | 0100 1101 | 77 | 4D |
| N | 0100 1110 | 78 | 4E |
| O | 0100 1111 | 79 | 4F |
| P | 0101 0000 | 80 | 50 |
| Q | 0101 0001 | 81 | 51 |
| R | 0101 0010 | 82 | 52 |
| S | 0101 0011 | 83 | 53 |
| T | 0101 0100 | 84 | 54 |
| U | 0101 0101 | 85 | 55 |
| V | 0101 0110 | 86 | 56 |
| W | 0101 0111 | 87 | 57 |
| X | 0101 1000 | 88 | 58 |
| Y | 0101 1001 | 89 | 59 |
| Z | 0101 1010 | 90 | 5A |


| Representation | Binary | Decimal | Hexadecimal |
|----------------|-----------|---------|-------------|
| a | 0110 0001 | 97 | 61 |
| b | 0110 0010 | 98 | 62 |
| c | 0110 0011 | 99 | 63 |
| d | 0110 0100 | 10 | 64 |
| e | 0110 0101 | 101 | 65 |
| f | 0110 0110 | 102 | 66 |
| g | 0110 0111 | 103 | 67 |
| h | 0110 1000 | 104 | 68 |
| i | 0110 1001 | 105 | 69 |
| j | 0110 1010 | 106 | 6A |
| k | 0110 1011 | 107 | 6B |
| l | 0110 1100 | 108 | 6C |
| m | 0110 1101 | 109 | 6D |
| n | 0110 1110 | 110 | 6E |
| o | 0110 1111 | 111 | 6F |
| p | 0111 0000 | 112 | 70 |
| q | 0111 0001 | 113 | 71 |
| E | 0111 0010 | 114 | 72 |
| s | 0111 0011 | 115 | 73 |
| t | 0111 0100 | 116 | 74 |
| u | 0111 0101 | 117 | 75 |
| v | 0111 0110 | 118 | 76 |
| w | 0111 0111 | 119 | 77 |
| x | 0111 1000 | 120 | 78 |
| y | 0111 1001 | 121 | 79 |
| z | 0111 1010 | 122 | 7A |

| Representation | Binary | Decimal | Hexadecimal |
|----------------|-----------|---------|-------------|
| 0 | 0011 0000 | 48 | 30 |
| 1 | 0011 0001 | 49 | 31 |
| 2 | 0011 0010 | 50 | 32 |
| 3 | 0011 0011 | 51 | 33 |
| 4 | 0011 0100 | 52 | 34 |
| 5 | 0011 0101 | 53 | 35 |
| 6 | 0011 0110 | 54 | 36 |
| 7 | 0011 0111 | 55 | 37 |
| 8 | 0011 1000 | 56 | 38 |
| 9 | 0011 1001 | 57 | 39 |

2. HD44780 communication

- Picture of time signals between ATmega328P and HD44780 (LCD keypad shield) when transmitting data **DE2**

DE2 = 0100 0100 – 0100 0101 – 0011 0010

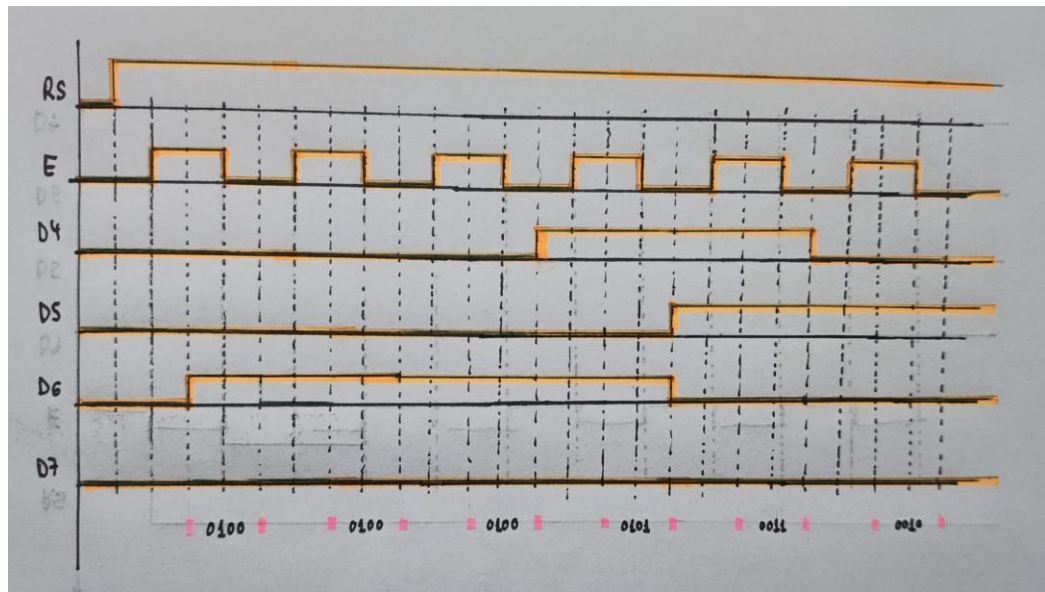

3. Stopwatch

- Listing of **TIMER2_OVF_vect** interrupt routine with complete stopwatch code (minutes:seconds.tenths) and square value computation

```
/**
 * ISR starts when Timer/Counter2 overflows. Update the stopwatch on
 * LCD display every sixth overflow, ie approximately every 100 ms
 * (6 x 16 ms = 100 ms).
 */
ISR(TIMER2_OVF_vect)
{
    static uint8_t number_of_overflows = 0;
    static uint8_t tens = 1;        // Tenths of a second
    static uint8_t secs = 0;        // Seconds
    static uint8_t mins = 0;        // Minutes

    char lcd_string[2] = " ";
    char lcd_sqr[2] = " ";

    number_of_overflows++;

    if (number_of_overflows >= 6)
    {
        // Do this every 6 x 16 ms = 100 ms
        number_of_overflows = 0;

        if(tens >= 10){

            tens = 0;

            secs++;

            /*SQUARE OF SECONDS*/
            itoa(secs*secs, lcd_sqr, 10);    // Convert decimal value to string
            lcd_gotoxy(COL2, 0);
            lcd_puts(lcd_sqr);

            /*SECONDS*/
            if (secs >= 10){
                itoa(secs, lcd_string, 10);    // Convert decimal value to string
                lcd_gotoxy(4, 0);
                lcd_puts(lcd_string);
            }else{
                itoa(secs, lcd_string, 10);    // Convert decimal value to string
                lcd_gotoxy(5, 0);
                lcd_puts(lcd_string);
            }
        }
    }
}
```

```

/*MINUTES*/
if (secs >= 60){
    secs = 0;

    itoa(secs, lcd_string, 10);    // Convert decimal value to string
    lcd_gotoxy(4, 0);
    lcd_puts(lcd_string);

    itoa(secs*secs, lcd_sqr, 10);    // Convert decimal value to string
    lcd_gotoxy(COL2, 0);
    lcd_puts(lcd_sqr);

    lcd_gotoxy(12, 0);
    lcd_data(0x20);
    lcd_gotoxy(13, 0);
    lcd_data(0x20);
    lcd_gotoxy(14, 0);
    lcd_data(0x20);

    mins++;

    if (mins >= 60){
        mins = 0;

        lcd_gotoxy(COL1, 0);
        lcd_putc('0');
        lcd_gotoxy(2, 0);
        lcd_putc('0');

    }else if (mins >= 10){
        itoa(mins, lcd_string, 10);    // Convert decimal value to string
        lcd_gotoxy(COL1, 0);
        lcd_puts(lcd_string);

    }else {
        itoa(mins, lcd_string, 10);    // Convert decimal value to string
        lcd_gotoxy(2, 0);
        lcd_puts(lcd_string);
    }

}

/*TENTHS*/
itoa(tens, lcd_string, 10);    // Convert decimal value to string
lcd_gotoxy(7, 0);
lcd_puts(lcd_string);

tens++;

}
}

```

You can find the code on my GitHub:

<https://github.com/GuicoRM/Digital-Electronics-2>

-
- The diagram illustrates the connection between an HD44780-1 LCD display and an ATmega328-2 microcontroller. The display shows the time '01:15.3' and the temperature '225'. The microcontroller's pins are connected to the display's RS, RW, and data pins. A 10k pull-down resistor is connected to the RS pin. The display's Vcc and Gnd pins are connected to the microcontroller's Vcc and Gnd pins, respectively. The display's D0-D7 pins are connected to the microcontroller's D0-D7 pins. The display's RS pin is connected to the microcontroller's D0 pin. The display's RW pin is connected to the microcontroller's D1 pin. The display's D4-D7 pins are connected to the microcontroller's D4-D7 pins. A 10k pull-down resistor is connected to the RS pin.

4. Progress bar

- Listing of **TIMER0_OVF_vect** interrupt routine with a progress bar

```
/**
 * ISR starts when Timer/Counter0 overflows. Shows
 * bar state, ie approximately every 100 ms
 * (6 x 16 ms = 100 ms).
 */
ISR(TIMER0_OVF_vect)
{
    static uint8_t symbol = 0;
    static uint8_t position = 0;

    lcd_gotoxy(COL1 + position, 1);
    lcd_putc(symbol);

    symbol++;

    if(symbol >= 6){
        symbol=0;
        position++;


        if (position>=10)
        {
            position=0;
            lcd_gotoxy(COL1, 1);
            lcd_puts("      ");
        }
    }
}
```

You can find the code on my GitHub:

<https://github.com/GuicoRM/Digital-Electronics-2>

- Screenshot of SimulIDE circuit when "Power Circuit" is applied

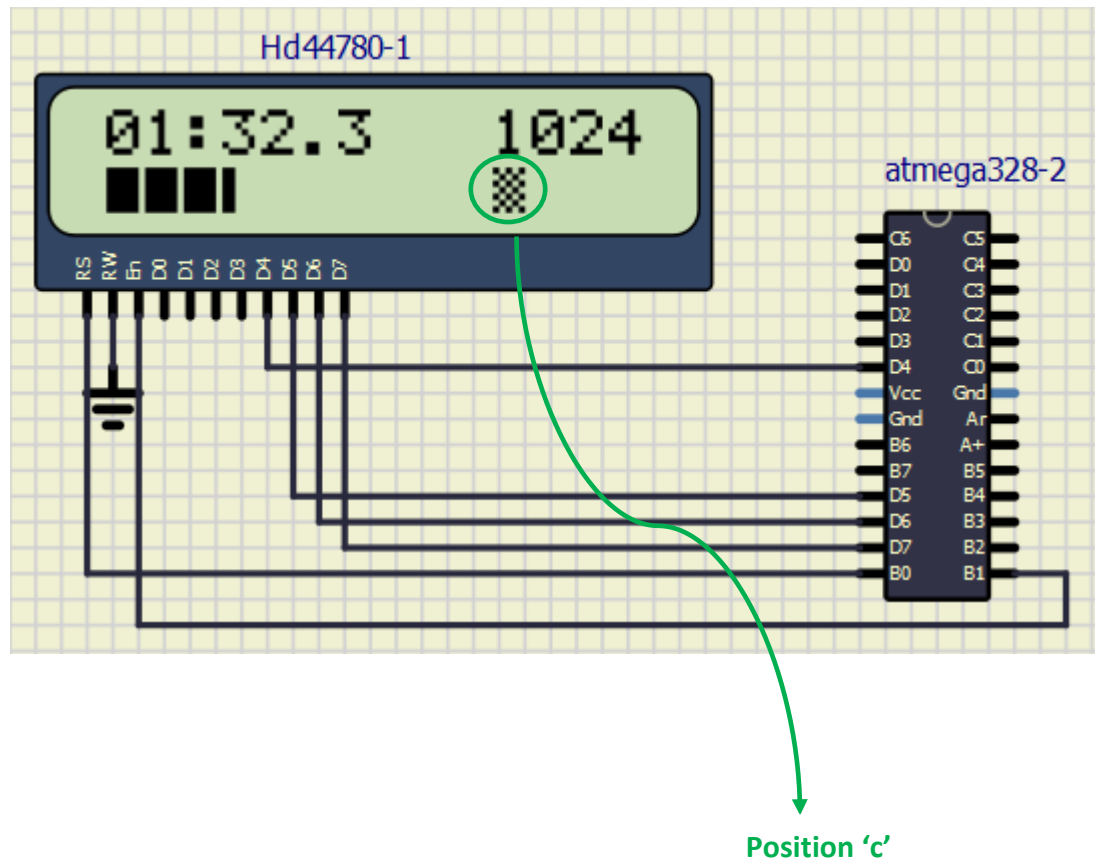Note: I also added one custome character ('chessboard') in position 'c' in order to test it



You can find the code of **custome character** on my GitHub:

<https://github.com/GuicoRM/Digital-Electronics-2>

5. EXTRA

- From the LCD position "c", displays running text, ie text that moves characters to the left twice per second

Note: I achieved to show moving text 'I like DE2!' in rudimentary way. It probably won't be the best way to get moving text, but it works.

```
/**
 * ISR starts when Timer/Counter1 overflows. Shows
 * 'I like DE2!', approximately two times per second
 */
ISR(TIMER1_OVF_vect)
{
    static uint8_t number_of_overflows = 0;
    static uint8_t h = 0;

    number_of_overflows++;

    lcd_gotoxy(COL2, 1);

    if (number_of_overflows >= 2)
    {
        number_of_overflows=0;

        if (h==0){
            lcd_puts(" lik");
            h++;
        }else if(h == 1){
            lcd_puts("like");
            h++;
        }else if(h == 2){
            lcd_puts("ike ");
            h++;
        }else if(h == 3){
            lcd_puts("ke D");
            h++;
        }
    }
}
```

```



    }else if(h == 4){
        lcd_puts("e DE");
        h++;
    }else if(h == 5){
        lcd_puts(" DE2");
        h++;
    }else if(h == 6){
        lcd_puts("DE2!");
        h++;
    }else if(h == 7){
        lcd_puts("E2! ");
        h++;
    }else if(h == 8){
        lcd_puts("2! ");
        h++;
    }else if(h == 9){
        lcd_puts("! ");
        h++;
    }else if(h == 10){
        lcd_puts(" ");
        h++;
    }else if(h == 11){
        lcd_puts(" I");
        h++;
    }else if(h == 12){
        lcd_puts(" I ");
        h++;
    }else if(h == 13){
        lcd_puts(" I l");
        h++;
    }else{
        h=0;
        lcd_puts("I li");
    }
}
}

```

You can find the code of **custome character** on my GitHub:

<https://github.com/GuicoRM/Digital-Electronics-2>

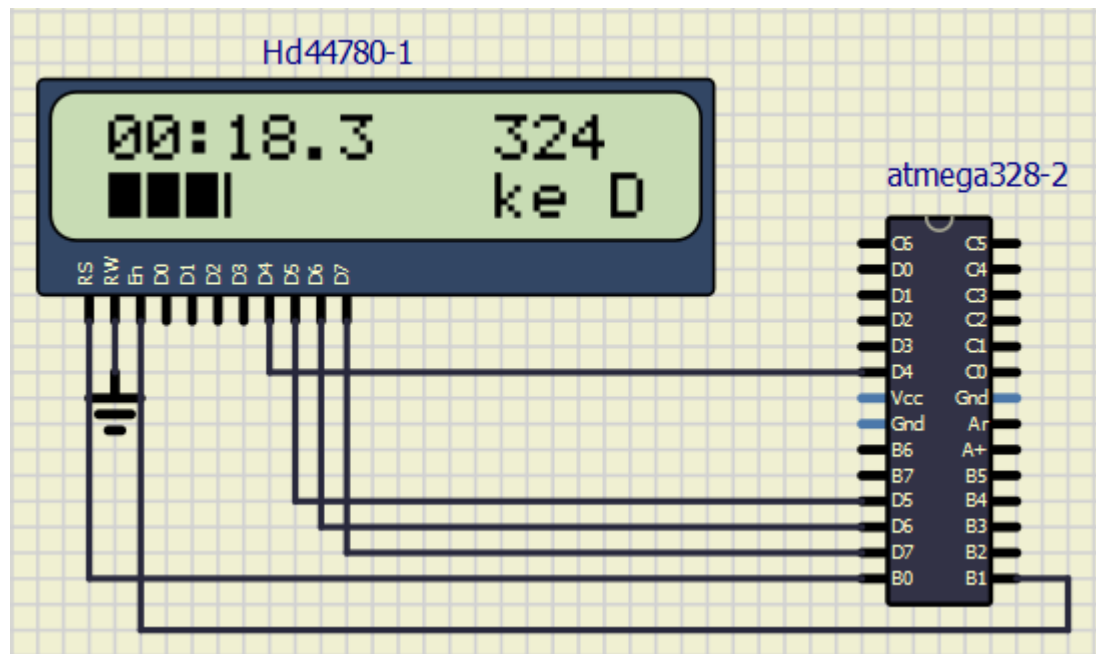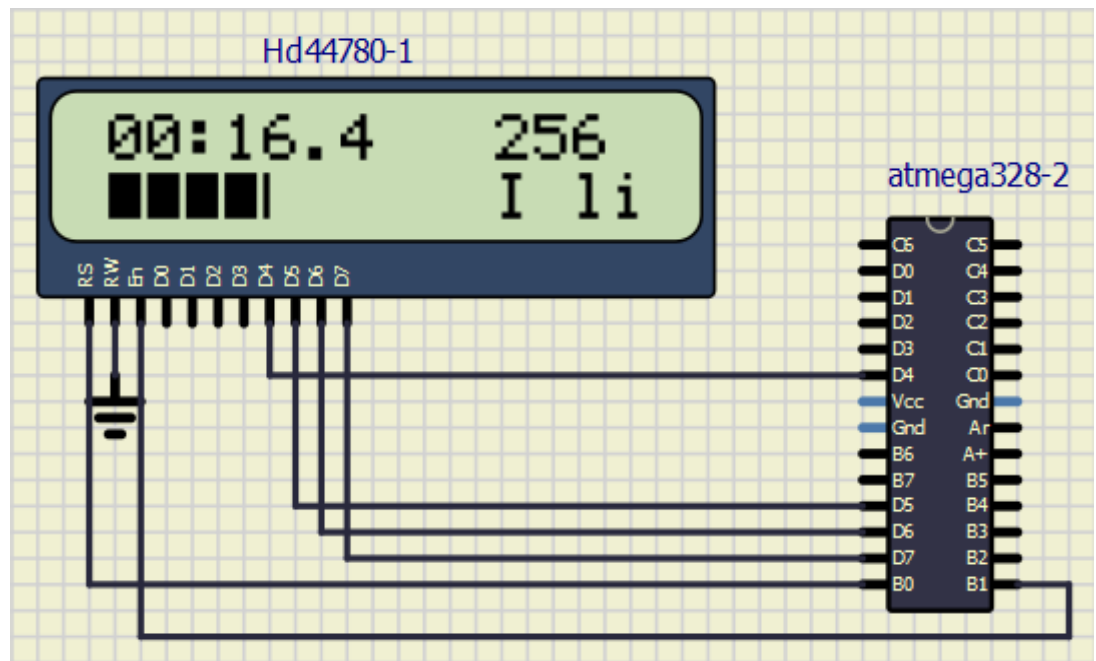- Screenshots of SimulIDE circuit when "Power Circuit" is applied



You can find the code of **custome character** on my GitHub:

<https://github.com/GuicoRM/Digital-Electronics-2>